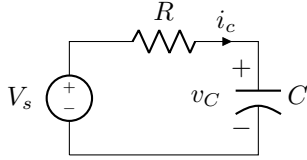


Lecture 25, Mar 16, 2022

Step Response of an RC Circuit

- What happens if we add an independent source to the RC circuit?



- - KVL gives: $-V_s + Ri_C + v_C = 0$
 - * $i_C = C \frac{dv_C}{dt} \implies -V_s + RC \frac{dv_C}{dt} + v_C(t) = 0 \implies \frac{dv_C}{dt} = \frac{-(v_C(t) - V_s)}{RC}$
 - * This is again separable: $\int \frac{1}{v_C(t) - V_s} dv_C = - \int \frac{1}{RC} dt$
 - $\implies \ln(v_C(t) - V_s) = -\frac{t}{RC} + K$
 - $\implies v_C(t) - V_s = Ae^{-\frac{t}{RC}}$
 - $\implies v_C(t) = Ae^{-\frac{t}{RC}} + V_s$
 - * Using the initial condition that $v_C(0^+) = V_0 \implies V_0 = A + V_s \implies A = V_0 - V_s$
 - * Finally, $v_C(t) = V_s + (V_0 - V_s)e^{-\frac{t}{RC}}$
 - As $t \rightarrow \infty$ we have $v_C(t) \rightarrow V_s$
 - At $t = 0$ there is a sharp corner as the voltage starts either increasing or decreasing and exponentially decaying to V_s
 - To find the current: $i_C(t) = C \frac{dv_C}{dt} = \frac{V_s - V_0}{R} e^{-\frac{t}{RC}}$
 - At $t = 0$ there is a discontinuity in the current as it jumps to $\frac{V_s - V_0}{R}$; as $t \rightarrow \infty, i_C \rightarrow 0$
 - In general $v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty))e^{-\frac{t}{RC}}$
 - This can also be applied to any general linear circuit connected to the capacitor by finding its Thevenin equivalent
 - The result can be broken down into two parts: a contribution from the initial voltage, and a part from the source: $v_C(t) = V_s(1 - e^{-\frac{t}{RC}}) + V_0 e^{-\frac{t}{RC}}$
 - The second part is exactly the behaviour of the source-free circuit
 - The first part is called the *forced response*, and the second part is the *natural response*